

# BUILD A CIRCUIT

Use devices below to create circuits. Draw wires to close circuits.

Simple Circuit

Parallel circuit

Complex Circuit

